

# In-semester Test I – Practice


- You will be provided with stub .hdl for each question.
- Do not change the names of the input or output pins. Only write code in the PARTS: area of the .hdl files
- Note that the practice test contains the solutions and test scripts
- During the real test you will not have access to the Internet, your handbook or previous files etc. You will be provided with the API for each of the gates.

## Instructions

- Download the test files from Minerva
- Extract the .zip
- The only files you need to modify are **q1.hdl**, **q2.hdl**, **q3.hdl**
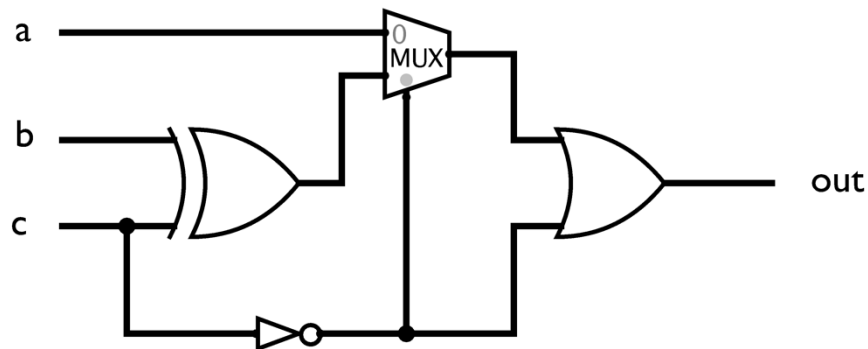
## Question I

Implement the following circuit in *q1.hdl*.



8 marks

## Question 2

Design a circuit that implements the following truth table in *q2.hdl*

a	b	c	out
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

8 marks

## Question 3

In *q3.hdl* implement a pattern detector. It takes in an 8-bit input. If the following pattern occurs in the bits, the output is 1. If the pattern does not occur, the output is 0. 'x' represents a don't care

x	x	1	0	0	1	x	x
---	---	---	---	---	---	---	---

For example, if the input was

1	1	1	0	0	1	0	0
---	---	---	---	---	---	---	---

then the output would be 1.

If the input was

1	1	0	0	0	1	0	0
---	---	---	---	---	---	---	---

then the output would be 0.

8 marks